



Figure 8.4 A circuit with three inputs, two additional sources that have assigned truth values, and one output.